

ELECTRICITY CELL ARRANGEMENT


PREPARED BY

TEACHER MAYANJA JOSEPH



LIGHT ACADEMY SECONDARY SCHOOL

CELL ARRANGEMENTS



1. Series arrangement

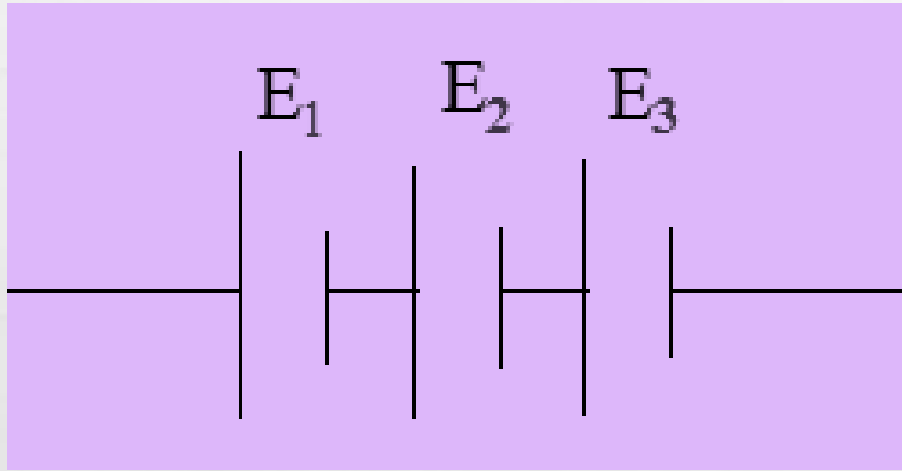
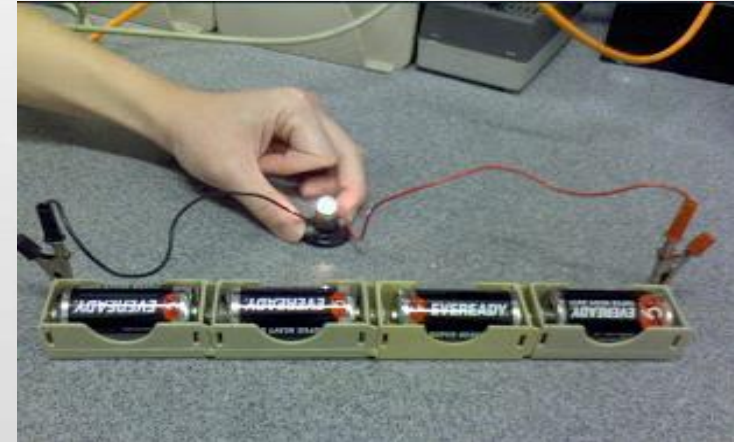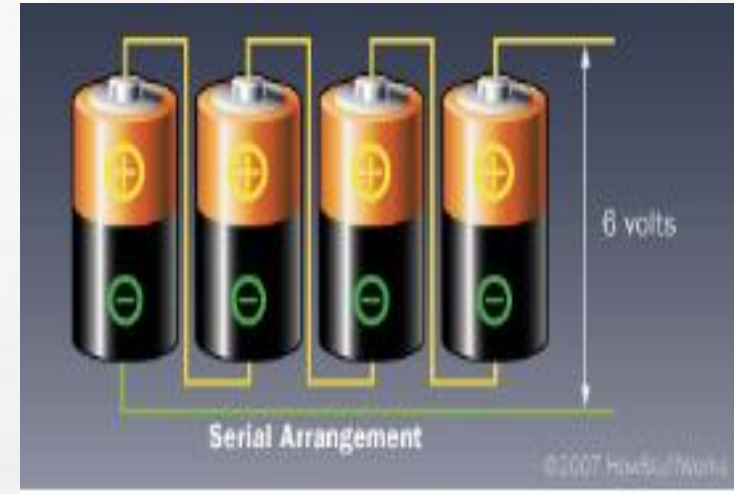
$$\text{Total } emf \ E = E_1 + E_2 + E_3$$



2. Parallel arrangement

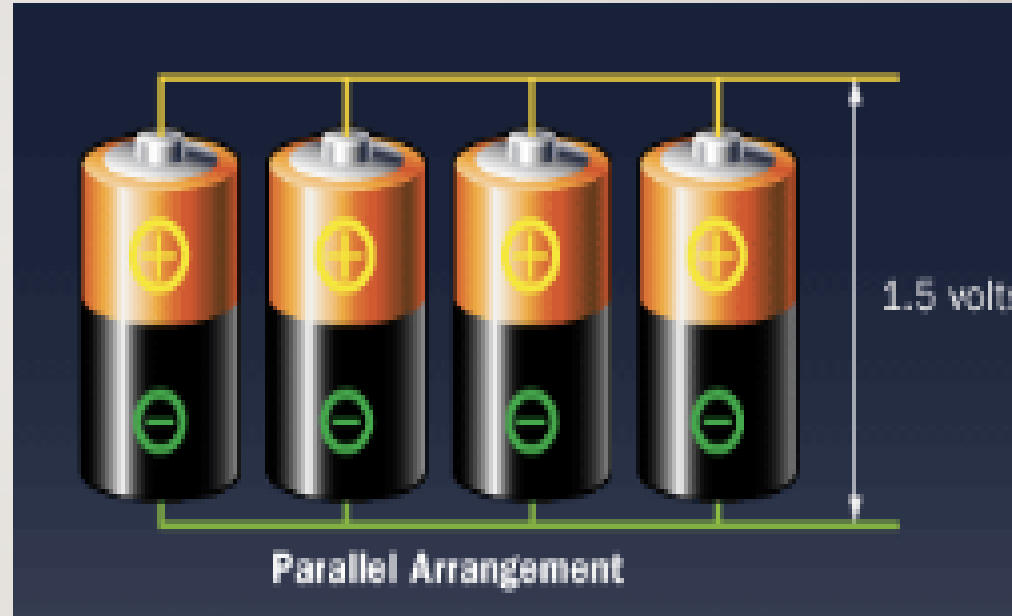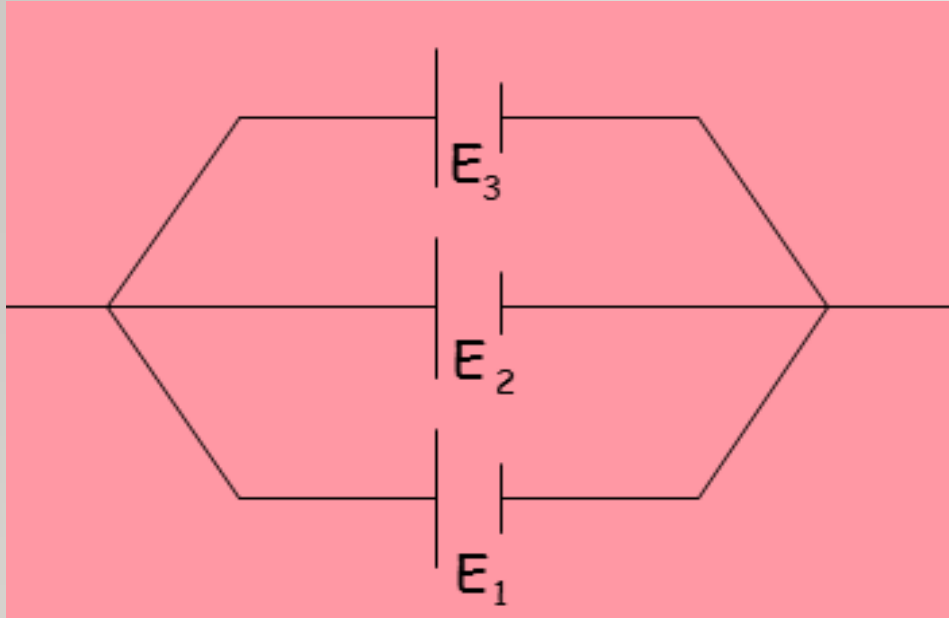

When cells of equal emf are connected in parallel

Total *emf* $E = E_1 = E_2 = E_3$


Advantages of series arrangement of cells over the parallel arrangement.

In series arrangement the **effective e.m.f** is greater than the **individual e.m.f** of the cells and hence a greater current is drawn from the series combination than in the parallel combination.

However the series arrangement has a disadvantage of all the cells being **drained at once** thus the cells have a shorter life span.

Example.

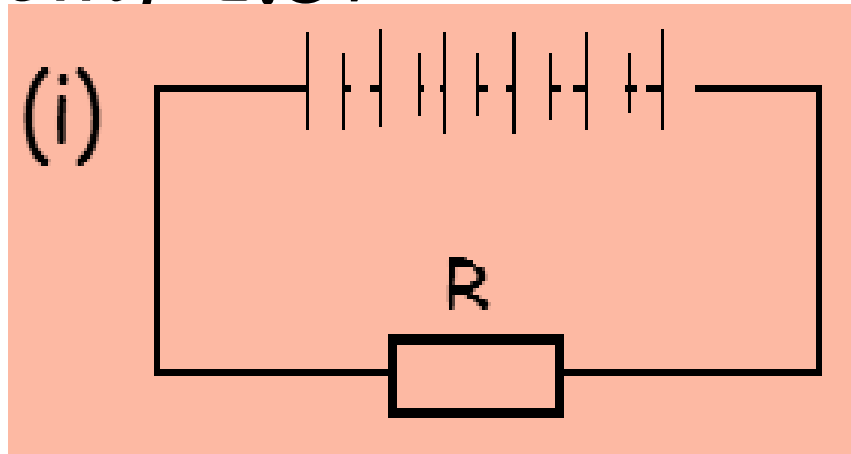
1. Find the total *emf* in each of the following circuits if each cell is of *emf* $1.5V$




Note: If the cells are connected in parallel and have internal resistance, their resistance is calculated as resistors in parallel.

EXAMPLES

1. Find the ammeter reading

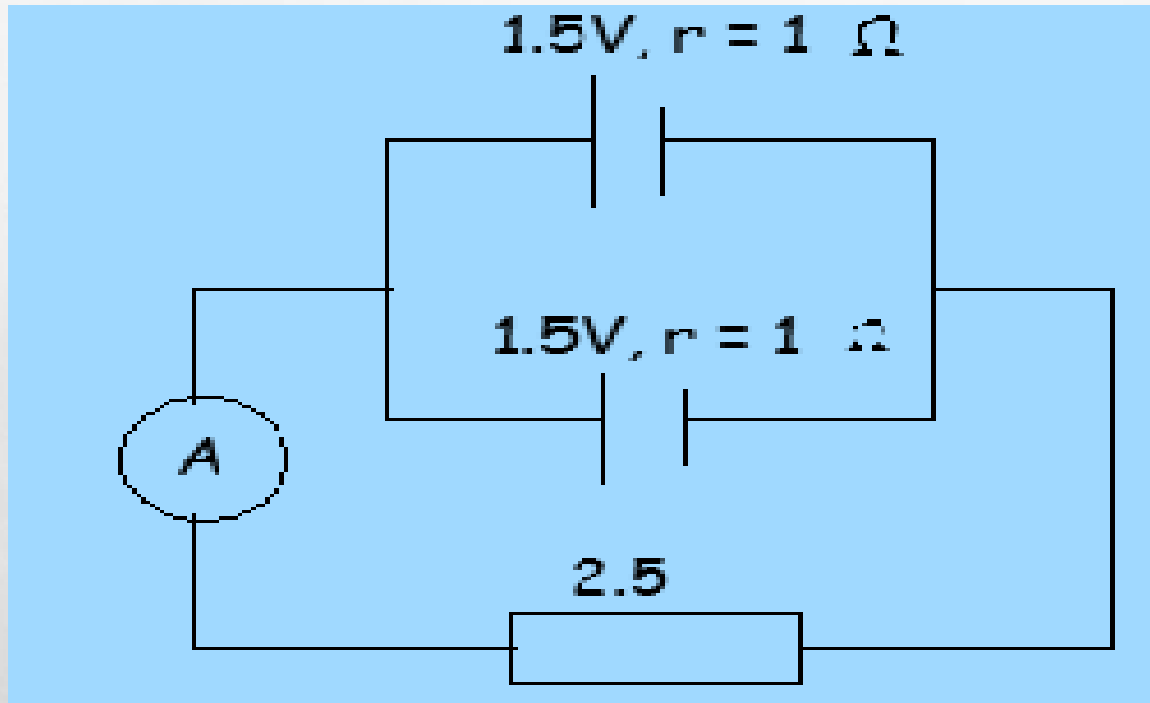

Example.

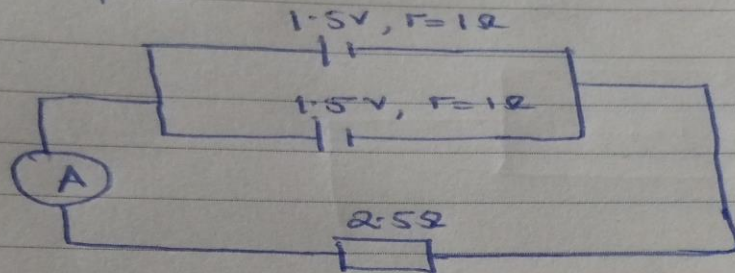

Find the ammeter reading.

$$E = 1.5V, \quad r = \frac{1 \times 1}{1 + 1} = 0.5\Omega$$

$$E = I(R + r)$$

$$1.5 = I(2.5 + 0.5)$$

$$1.5 = I(3)$$

$$I = \frac{1.5}{3} = \underline{\hspace{1cm}} A$$

$$= \frac{3}{2} \div 3$$

$$= \frac{3}{2} \times \frac{1}{3}$$

$$= \underline{\underline{0.5A}}$$

2. A battery containing 8 cells each of *emf* 1.5V and internal resistance 0.5Ω is connected to two other resistors of 4Ω and 16Ω . Calculate the minimum and maximum current that can flow through the battery.

You can the link below

<https://youtu.be/dgkaE7eiY5w>



Prepared by
Teacher Mayanja joseph
Light academy secondary school

e-light platform

